

Capacitors – 2021/20 GCE Physics A Component 02**1. Nov/2021/Paper_H556_02/No.6**

A student is modelling the decay of charge for a capacitor discharging through a resistor using the equation $\frac{\Delta Q}{\Delta t} = -0.2Q$.

The student decides to use $\Delta t = 0.5 \text{ s}$.

The initial charge on the capacitor is $1000 \mu\text{C}$.

Part of the modelling spreadsheet from the student is shown below.

t/s	Charge Q left on capacitor at time $t/\mu\text{C}$	Charge ΔQ decaying in the next $0.5 \text{ s}/\mu\text{C}$
0	1000	100
0.5	900	
1.0		
1.5		

What is the value of Q in μC at $t = 1.5 \text{ s}$?


- A** 700
- B** 720
- C** 729
- D** 800

Your answer

[1]

2. Nov/2021/Paper_H556_02/No.20

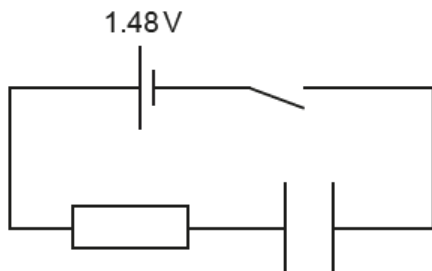(a) The diagram below shows a circuit to charge a capacitor.




The electromotive force (e.m.f.) E of the cell is 1.48 V and it has negligible internal resistance. The resistance of the resistor is $120\text{ k}\Omega$ and the capacitance of the capacitor is $2000\text{ }\mu\text{F}$. At time $t = 0$ the capacitor is uncharged. The switch is closed at time $t = 0$.

Calculate the time t when the potential difference across the capacitor is 1.00 V .

$t = \dots\dots\dots\text{ s [4]}$

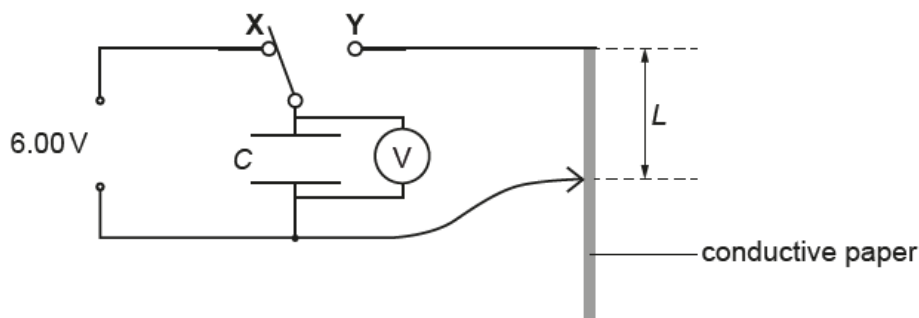(b) A capacitor of capacitance C is connected across a strip of conductive paper.



The switch is moved from **X** to **Y**, and the time t for the potential difference across the capacitor to halve is measured.

The time t is given by the expression


$$t = (Ck \ln 2) \times L$$

where k is the resistance of the conductive paper per unit length and L is the length of the conductive paper.

The value of C is $1.2 \times 10^{-3} \text{ F}$.

In an experiment, L is changed and t measured.

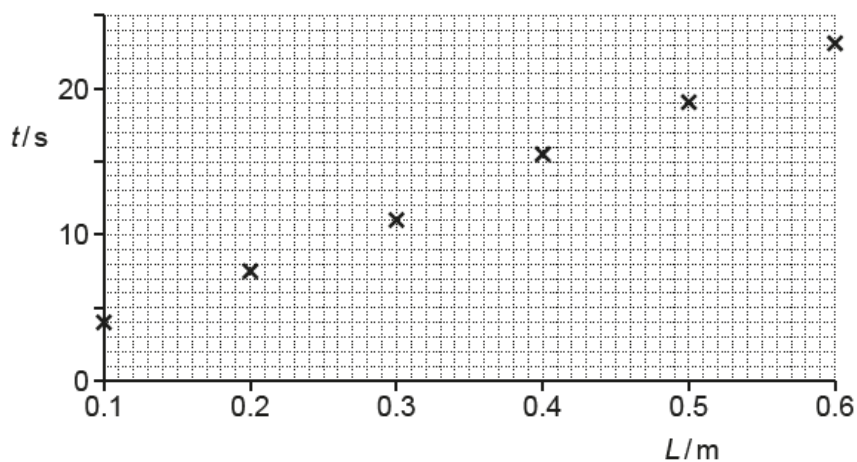The data points are plotted on a t against L grid as shown below.




Draw a straight line of best fit through the data points, and use the gradient of this line to determine k .

$$k = \dots\dots\dots \Omega \text{ m}^{-1} \text{ [4]}$$

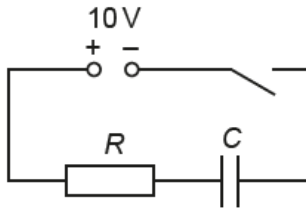3. Nov/2020/Paper_H556_02/No.7

The diagram below shows a circuit used to charge a capacitor.



The power supply has electromotive force (e.m.f.) 10 V and negligible internal resistance.

The capacitor has capacitance C and the resistor has resistance R .

The switch is closed at time $t = 0$.

The table below shows potential difference V across the resistor at various values of time t .

V/V	10	6.3	5.0	3.7
t/s	0	2.8	4.2	6.0

What is the product $C \times R$ for this circuit?

- A 0 s
- B 2.8 s
- C 4.2 s
- D 6.0 s

Your answer

[1]

4. Nov/2020/Paper_H556_02/No.8

A capacitor discharges through a resistor.

At time $t = 0$ the potential difference V across the capacitor is V_0 .

At time $t = 2.0$ s, $V = 0.90 V_0$.

Which statement is **not** correct?

- A At $t = 4.0$ s, $V = 0.81 V_0$.
- B The capacitor is fully discharged after $t = 10$ s.
- C The potential difference across the resistor is the same as that for the capacitor.
- D The potential difference V decreases exponentially with time t .


Your answer

[1]

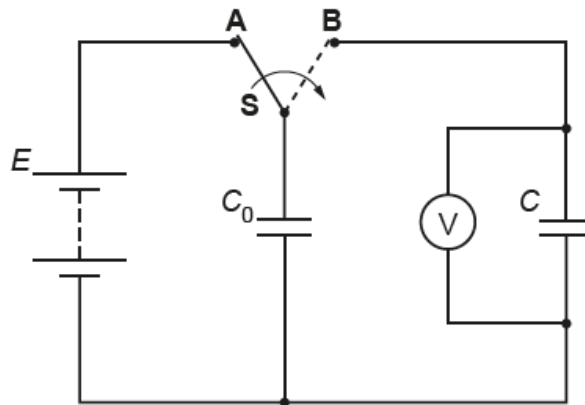5. Nov/2020/Paper_H556_03/No.2

The diagram below shows a circuit containing two capacitors which are both initially uncharged. The battery has e.m.f. E and negligible internal resistance.

The switch **S** is first moved to position **A** until the capacitor of capacitance C_0 is fully charged.



The switch **S** is then moved to position **B**. The initial charge stored by the capacitor of capacitance C_0 is shared between the two capacitors. The final reading on the voltmeter is V .

(a) Show that $V = \frac{C_0}{C + C_0} E$.

[2]


- (b) A student wants to determine the values of E and C_0 by repeating the experiment above and measuring the potential difference (p.d.) V for a selection of capacitors of capacitance C .

The student decides to plot a graph of $\frac{1}{V}$ against C .

- (i) Use the expression in (a) to show that the graph should be a straight line of gradient $\frac{1}{C_0 E}$ and y-intercept $\frac{1}{E}$.

[1]

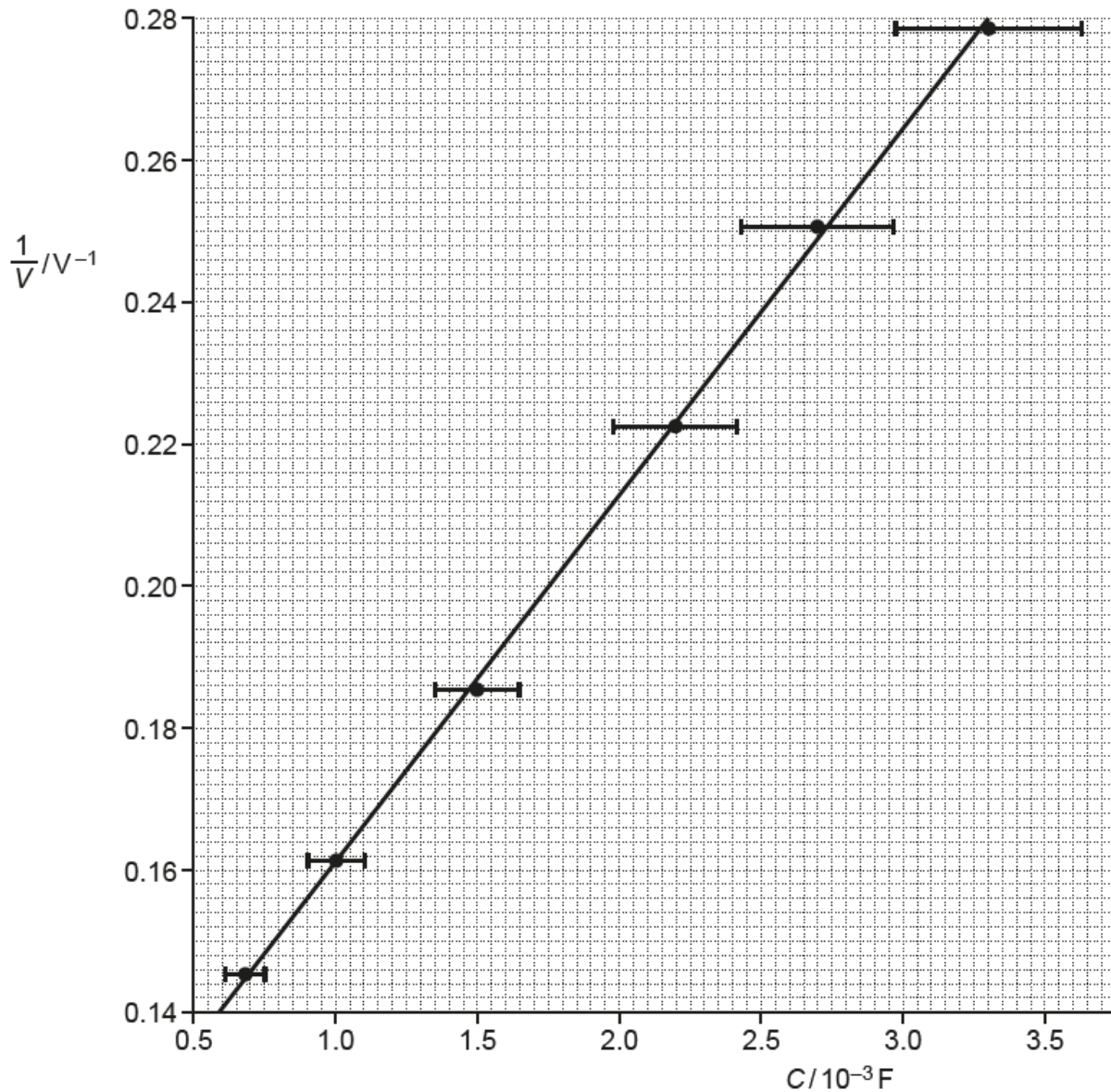- (ii) The data points, error bars and the line of best fit drawn by the student are shown in the graph below.



The gradient of the line of best fit is $51 \text{ V}^{-1} \text{ F}^{-1}$. The value of E is 9.1 V .

Determine the value of C_0 in millifarads (mF). Write your answer to 2 significant figures.

$C_0 = \dots\dots\dots \text{ mF [2]}$

(iii) Draw on the graph a straight line of worst fit.

Use this line to determine the absolute uncertainty in your value of C_0 . Write your answer to an appropriate number of significant figures.

absolute uncertainty = mF [4]

(c) The experiment is repeated with a resistor of resistance $10\text{ k}\Omega$ placed in series between **S** and the capacitor of capacitance C_0 .

State with a reason what effect, if any, this would have on the experiment.

.....

 [1]